

WORKED EXAMPLES

1.15 Find the p.d. between the points X and Y in the network shown in Fig. 1.24

Soln.: Let I_1 and I_2 be the loop currents.

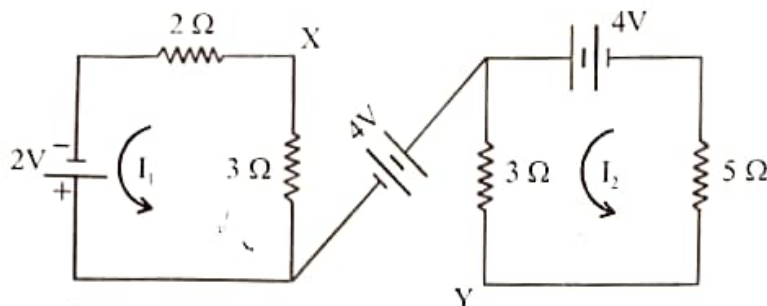


Fig. 1.24

$$I_1 = \frac{2}{2+3} = 0.4 \text{ A} \quad \text{and} \quad I_2 = \frac{4}{3+5} = 0.5 \text{ A}$$

$$\begin{aligned} \therefore V_{XY} &= +3 I_2 - 4 - 3 I_1 = 3 \times 0.5 - 4 - 3 \times 0.4 \\ &= -3.7 \text{ volts (Y is at a higher potential than X)} \end{aligned}$$

1.16 In the network shown in Fig. 1.25 determine the direction and magnitude of current flow in the milli-ammeter A, having a resistance of 10Ω .

Soln.: Let the current distribution be as shown in Fig. 1.25.

$$\text{For abda} \quad -4 - 10 I_2 + 100 (I_1 - I_2) = 0$$

$$\text{i.e.} \quad 100 I_1 - 110 I_2 = 4 \quad (\text{i})$$

$$\text{For bcdb} \quad -2 + 25 I_1 + 10 I_2 = 0$$

$$\text{i.e.} \quad 25 I_1 + 10 I_2 = 2 \quad (\text{ii})$$

Solving (i) and (ii), we get

$$I_2 = \frac{\begin{vmatrix} 100 & 4 \\ 25 & 2 \end{vmatrix}}{\begin{vmatrix} 100 & -110 \\ 25 & 10 \end{vmatrix}} = 0.0267 \text{ A} = 26.7 \text{ mA}$$

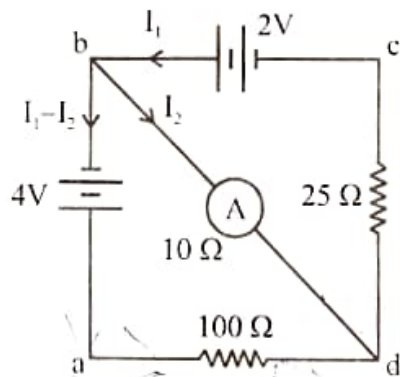


Fig. 1.25

1.17 In the network shown in Fig. 1.26, find the current flowing in each branch using Kirchhoff's laws.

Soln.: Assume the currents as shown.

$$\text{For ABDA,} \quad -10 I_2 - 25 I_3 + 20 (I_1 - I_2) = 0$$

$$\text{i.e.} \quad 4 I_1 - 6 I_2 - 5 I_3 = 0 \quad (1.29)$$

$$\text{For BCDB,} \quad -15 (I_2 - I_3) + 5 (I_1 - I_2 + I_3) + 25 I_3 = 0$$

$$\text{i.e. } I_1 - 4 I_2 + 9 I_3 = 0 \quad (1.30)$$

$$\text{For } ABCFEA, -20(I_1 - I_2) - 5(I_1 - I_2 + I_3) + 150 = 0$$

$$\text{i.e. } 5 I_1 - 5 I_2 + I_3 = 30 \quad (1.31)$$

Solving equations (1.29), (1.30) and (1.31), we get

$$I_1 = \begin{vmatrix} 0 & -6 & -5 \\ 0 & -4 & 9 \\ 30 & -5 & 1 \end{vmatrix} = 12.7 \text{ A}, \quad I_2 = \begin{vmatrix} 4 & 0 & -5 \\ 1 & 0 & 9 \\ 5 & 30 & 1 \end{vmatrix} = 7.03 \text{ A}$$

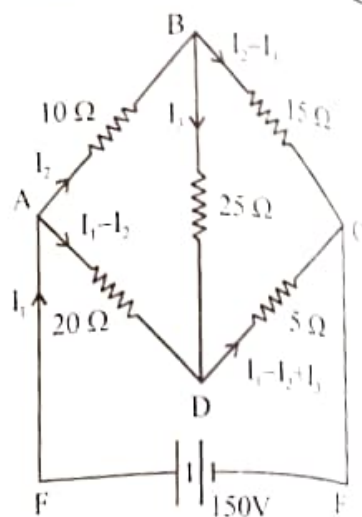


Fig. 1.26

Substituting I_1 and I_2 in equations (1.29), we get $I_3 = 1.72 \text{ A}$

The various branch currents are :

$$I_{AB} = I_1 = 12.7 \text{ A}, \quad I_{BC} = I_2 = 7.03 \text{ A}, \quad I_{BD} = I_3 = 1.72 \text{ A}$$

$$I_{DC} = I_1 - I_2 + I_3 = 12.7 - 7.03 + 1.72 = 7.39 \text{ A}, \quad I_{AD} = I_1 - I_2 = 12.7 - 7.03 = 5.67 \text{ A}$$

$$I_{CEFA} = I_1 = 12.7 \text{ A}$$

- 1.18 In the circuit shown in Fig. 1.27, what is the voltage across cd if (i) switch S is open and (ii) switch S is closed.

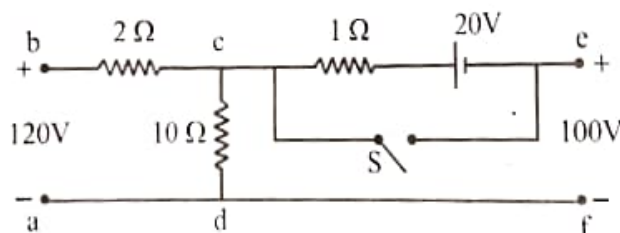


Fig. 1.27

Soln.: i) When S is open, the circuit is written as below.

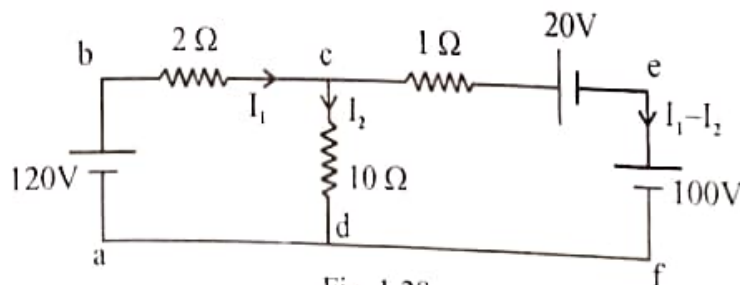


Fig. 1.28

The current distribution is as shown in Fig. 1.28

$$\text{For } abcda, \quad 120 - 2 I_1 - 10 I_2 = 0, \quad \text{i.e. } I_1 + 5 I_2 = 60 \quad (1.32)$$

$$\text{For } dcefd \quad 10 I_2 - 1 (I_1 - I_2) - 20 - 100 = 0$$

$$\text{i.e. } -I_1 + 11 I_2 = 120 \quad (1.33)$$

Solving equations (1.32) and (1.33), we get

$$I_1 = 3.75 \text{ A} \quad \text{and} \quad I_2 = 11.25 \text{ A}$$

$$\text{Voltage across cd} = V_{cd} = 10 \times I_2 = 10 \times 11.25 = 112.5 \text{ V}$$

- ii) When the switch S is closed, no current flows through 1Ω and 20 V . The resulting circuit is as shown below.

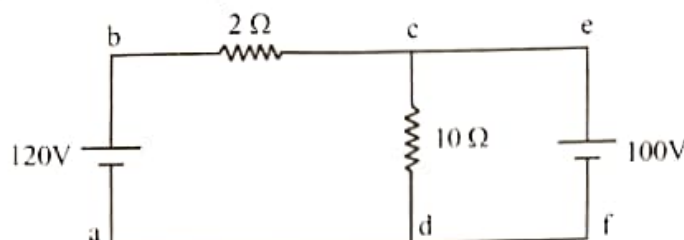


Fig. 1.29

$$\therefore V_{cd} = 100 \text{ V}$$

- 1.19 Find the currents in the various branches of the given network shown in Fig.1.30**

Soln.: The currents are distributed in the various branches as shown

For ABCDEFA

$$\begin{aligned} & -0.02 I - 0.02 (I - 80) - 0.03 (I + 10) \\ & - 0.02 (I - 140) - 0.01 (I - 20) - 0.01 (I - 100) = 0 \end{aligned}$$

On solving, we get, $I = 48.18 \text{ A}$.

$$\therefore I_{AB} = I = 48.18 \text{ A}$$

$$I_{BC} = (I - 80) = -31.82 \text{ A} \quad \text{or} \quad I_{CB} = 31.82 \text{ A}$$

$$I_{CD} = (I + 10) = 58.18 \text{ A}$$

$$I_{DE} = (I - 140) = -91.82 \text{ A} \quad \text{or} \quad I_{ED} = 91.82 \text{ A}$$

$$I_{EF} = (I - 20) = 28.18 \text{ A}$$

$$I_{FA} = (I - 100) = -51.82 \text{ A} \quad \text{or} \quad I_{AF} = 51.82 \text{ A}$$

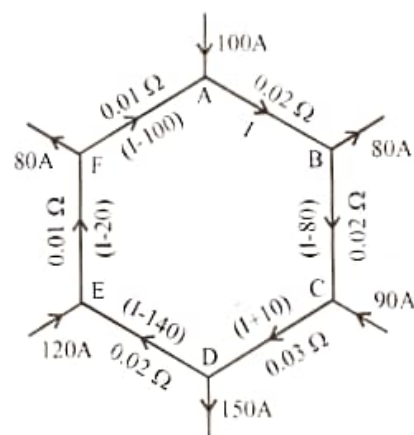


Fig. 1.30

- 1.20 Find the currents I_1 , I_2 and I_3 and the voltages V_a , V_b in the network shown in Fig.1.31.**

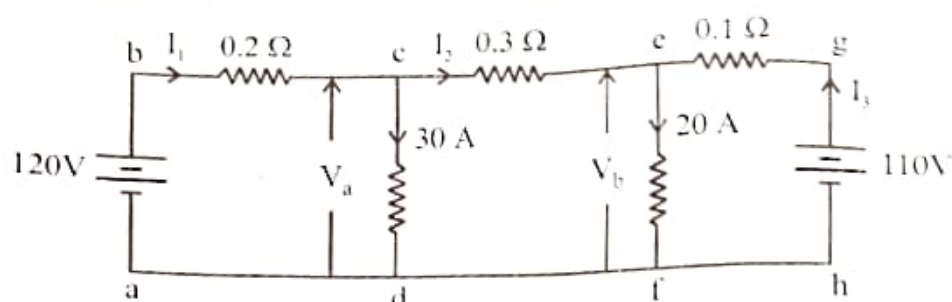


Fig. 1.31

Soln. : From the circuit, we know

$$I_2 = I_1 - 30, \quad I_3 + I_1 - 30 = 20 \quad \text{i.e.} \quad I_3 = 50 - I_1$$

For abcghfda, $120 - 0.2 I_1 - 0.3 I_2 + 0.1 I_3 - 110 = 0$

Substituting for I_2 and I_3 , we get

$$-0.6 I_1 = -24 \quad \text{or} \quad I_1 = 40 \text{ A}$$

$$\therefore I_2 = 40 - 30 = 10 \text{ A}, \quad I_3 = 50 - 40 = 10 \text{ A}$$

$$V_a = 120 - 0.2 \times 40 = 112 \text{ V}, \quad V_b = 110 - 0.1 \times 10 = 109 \text{ V}$$

1.21 For the following network shown in Fig. 1.32, find the currents in all the branches and potential difference across AD and CE.

Soln.: The currents are distributed as shown in the figure.1.32.

For the loop ABCDEA,

$$-2.5 I - (I + 10) \times 1 - 2(I + 19) - 3(I + 17) - 4(I + 22) = 0$$

$$\text{i.e.} \quad I = -14.96 \text{ A}$$

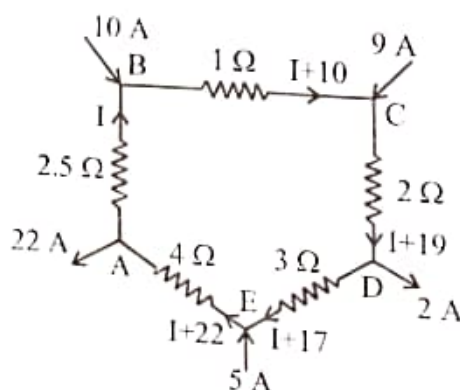


Fig. 1.32

$$\therefore I_{AB} = I = -14.96 \text{ A}$$

$$\text{i.e.} \quad I_{BA} = 14.96 \text{ A}$$

$$I_{BC} = I + 10 = -14.96 + 10 = -4.96 \text{ A}$$

$$\text{i.e.} \quad I_{CB} = 4.96 \text{ A}$$

$$I_{CD} = I + 19 = -14.96 + 19 = 4.04 \text{ A}$$

$$I_{DE} = I + 17 = -14.96 + 17 = 2.04 \text{ A}$$

$$I_{EA} = 1 + 22 = -14.96 + 22 = 7.04 \text{ A}$$

$$V_{AD} = -3(1 + 17) - 4(1 + 22) = -3 \times 2.04 - 4(7.04) = -34.28 \text{ V}$$

$$V_{CE} = 3(1 + 17) + 2(1 + 19) = 3 \times 2.04 + 2(4.04) = 14.2 \text{ V}$$

- 1.22** The current in the 6Ω resistance of the network shown in the Fig. 1.33 is 2A. Determine the currents in all the branches and the applied voltage.

Soln. : Let I be the total current.

$$\text{Then, } 2 = I \times \frac{8}{8+6}$$

$$\text{i.e. } I = 3.5 \text{ A}$$

$$\therefore I_2 = I - 2 = 3.5 - 2 = 1.5 \text{ A}$$

$$I_1 = 3.5 \times \frac{20}{20+8} = 2.5 \text{ A}$$

$$I_3 = I - I_1 = 3.5 - 2.5 = 1 \text{ A}$$

$$V = 4 \times I + 6 \times 2 + 8 \times I_1 = 4 \times 3.5 + 6 \times 2 + 8 \times 2.5 = 46 \text{ V}$$

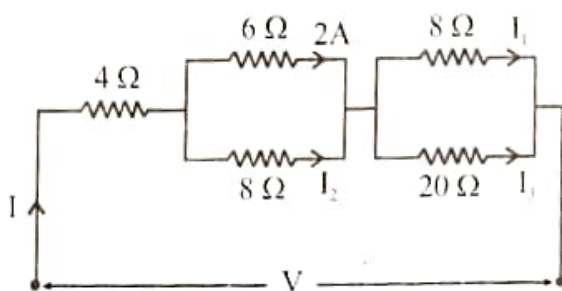


Fig. 1.33

- 1.23** The circuit in Fig.1.33(a) shows a hollow cube of 12 wires, each having a resistance of r . Find the resistance between any two diagonally opposite corners.

Soln.: Let a current $6I$ enter at a . Because of the symmetry of the cube, the current distribution in the wires is as shown in the Fig.1.34. A current $6I$ leaves the diagonally opposite corner g . Let a battery of E volts be connected between a and g . Then, applying Kirchhoff's voltage law for the closed path $aefga$, we get

$$E = r(2I + I + 2I) = 5Ir$$

If R is the equivalent resistance between a and g , then $E = 6IR$.

$$\therefore 5Ir = 6IR \quad \text{or} \quad R = \frac{5}{6} r.$$

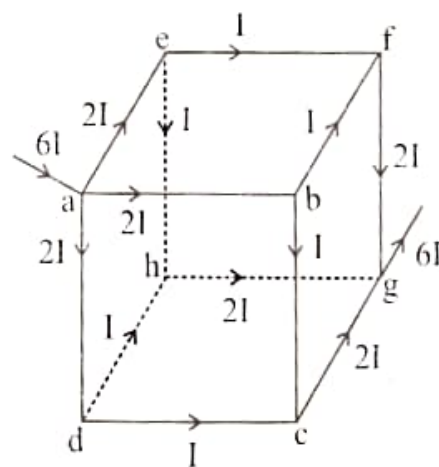


Fig.1.34

- 1.24** Find the current in the various branches of the circuit shown in Fig.1.35.

Soln.: The current distribution in the various branches of the circuit is as shown in the Fig.1.35.

For the loop $abdefa$:

$$-2I_1 - 5(I_1 - I_2) - 8(I_1 - I_2 + I_3) + 10 = 0$$

$$\text{i.e. } 15I_1 - 13I_2 + 8I_3 = 10 \quad \text{--- (1)}$$

For the loop bedb:

$$-4I_2 - 6I_3 + 5(I_1 - I_2) = 0$$

$$\text{i.e. } 5I_1 - 9I_2 - 6I_3 = 0 \quad \text{--- (2)}$$

For the loop cdec:

$$-6I_3 - 8(I_1 - I_2 + I_3) + 10(I_2 - I_3) = 0$$

$$\text{i.e. } 4I_1 - 9I_2 - 12I_3 = 0 \quad \text{--- (3)}$$

Solving equations (1), (2) and (3), we get

$$I_1 = 2 \text{ A}, \quad I_2 = 1.33 \text{ A} \quad \text{and} \quad I_3 = -1.59 \text{ A}.$$


The currents in the various branches are:

$$I_{efab} = I_1 = 2 \text{ A}, \quad I_{bc} = I_2 = 1.33 \text{ A}, \quad I_{cd} = I_3 = -1.59 \text{ A} \quad \text{i.e. } I_{dc} = 1.59 \text{ A},$$

$$I_{bd} = I_1 - I_2 = 2 - 1.33 = 0.67 \text{ A}$$

$$I_{ce} = I_2 - I_3 = 1.33 - (-1.59) = 2.92 \text{ A}$$
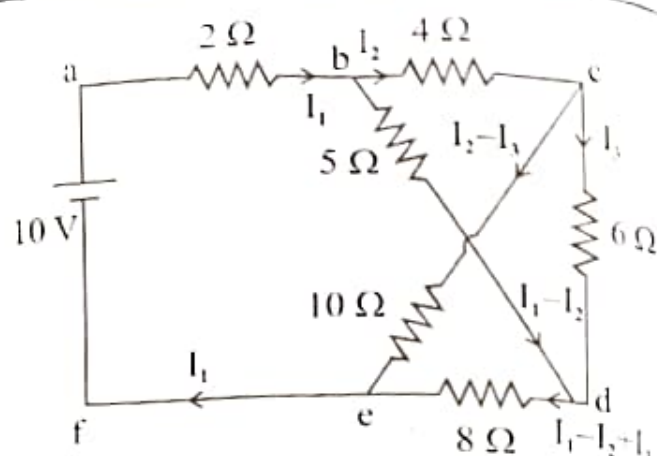
$$I_{de} = I_1 - I_2 + I_3 = 2 - 1.33 - 1.59 = -0.92 \text{ A} \quad \text{i.e. } I_{ed} = 0.92 \text{ A}$$



WORKED EXAMPLES

1.1 Two resistances $20\ \Omega$ and $40\ \Omega$ are connected in parallel. A resistance of $10\ \Omega$ is connected in series with the combination. A voltage of 200 V is applied across the circuit. Find the current in each resistance and the voltage across $10\ \Omega$. Find also the power consumed in all the resistances.

Soln. : The total resistance of the circuit is given by

$$R = 10 + \frac{20 \times 40}{20 + 40} = 23.33\ \Omega$$

$$I = \frac{200}{23.33} = 8.57\text{ A}$$

$$I_1 = 8.57 \times \frac{40}{40 + 20} = 5.71\text{ A}$$

$$I_2 = 8.57 - 5.71 = 2.86\text{ A}, \quad V_{10\Omega} = 8.57 \times 10 = 85.7\text{ volts}$$

$$P_{10\Omega} = 8.57^2 \times 10 = 734.45\text{ watts}, \quad P_{20\Omega} = 5.71^2 \times 20 = 652.08\text{ watts}$$

$$P_{40\Omega} = 2.86^2 \times 40 = 327.18\text{ watts}$$

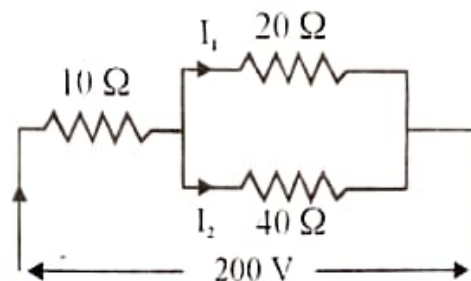


Fig.1.8

1.2 A D.C. arc has a voltage current relation given by $V = 20 + \frac{40}{I}$. It is connected in series with a resistor. The total voltage applied is 120 V. If the voltage across the arc is half the voltage across the resistor, find the value of the resistor.

Soln.: For the arc, $40 = 20 + \frac{40}{I}$,

$$\therefore I = 2 \text{ A}$$

for the resistor $I R = 80$ i.e. $2 R = 80$

$$\therefore R = 40 \Omega$$

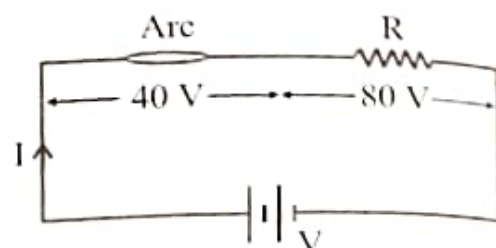


Fig. 1.9

1.3 Three resistors A, B and C are connected in parallel taking a total current of 12 A from the supply. If $I_B = 2 I_A$, $I_C = 3.5 I_B$ and total power drawn is 3 kW, calculate (a) current drawn by each resistor (b) supply voltage and (c) power consumed by each resistance.

Soln.: (a) $I_A + I_B + I_C = I = 12 \text{ A}$

$$I_A + 2 I_A + 3.5 I_B = 12$$

$$3 I_A + 3.5 (2 I_A) = 12$$

$$\therefore I_A = 1.2 \text{ A}, I_B = 2.4 \text{ A} \text{ and } I_C = 8.4 \text{ A}$$

(b) $P = 3,000 \text{ W} = V I$

$$\therefore V = \frac{3000}{12} = 250 \text{ V}$$

(c) $P_A = 250 \times 1.2 = 300 \text{ watts}$

$$P_B = 250 \times 2.4 = 600 \text{ watts,}$$

$$P_C = 250 \times 8.4 = 2,100 \text{ watts}$$

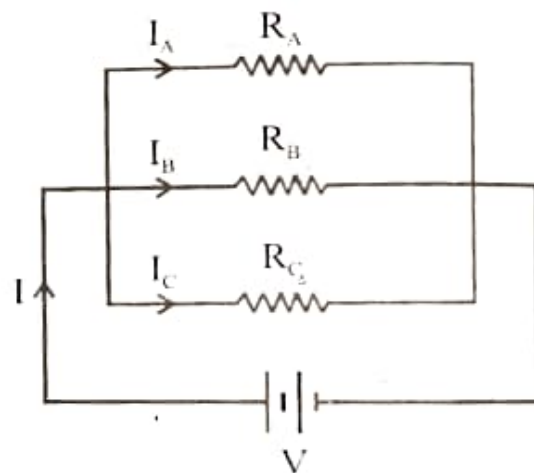


Fig. 1.10

1.4 In the series parallel circuit shown in Fig. 1.11, find (i) the voltage drop across 4Ω resistor and (ii) the supply voltage.

Soln.: Let current I , I_1 and I_2 flow in the branches as shown in the Fig. 1.11

$$I_1 = \frac{50}{10} = 5 \text{ A}, \quad I_2 = \frac{50}{8} = 6.25 \text{ A}$$

$$I = I_1 + I_2 = 5 + 6.25 = 11.25 \text{ A}$$

$$\text{i) } V_{4\Omega} = 11.25 \times 4 = 45 \text{ V}$$

$$\text{ii) } 24 \Omega \parallel 12 \Omega = \frac{24 \times 12}{24 + 12} = 8 \Omega$$

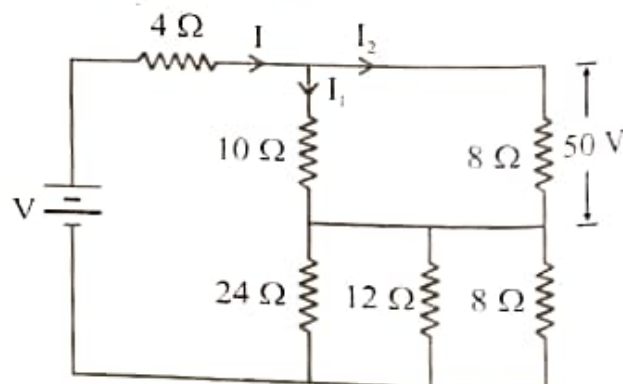


Fig. 1.11

$$8 \Omega \parallel 8 \Omega = \frac{8 \times 8}{8 + 8} = 4 \Omega, \quad 10 \Omega \parallel 8 \Omega = \frac{10 \times 8}{10 + 8} = 4.44 \Omega$$

$$\text{Total resistance} = R = 4 + 4.44 + 4 = 12.44 \Omega$$

$$\text{Supply voltage} = V = 12.44 \times I = 12.44 \times 11.25 = 140 \text{ volts}$$

1.5 A resistance R is connected in series with a parallel circuit comprising 20 Ω and 48 Ω . The total power dissipated in the circuit is 1,000 W and the applied voltage is 250 V. Calculate R.

$$\text{Soln.: } P = \frac{V^2}{R_T} = \frac{250^2}{R_T} = 1,000$$

$$\therefore R_T = \text{total resistance} = \frac{250^2}{1,000} = 62.5 \Omega$$

$$R_T = R + \frac{20 \times 48}{20 + 48} \quad \text{i.e.} \quad 62.5 = R + 14.12$$

$$\therefore R = 48.38 \Omega$$

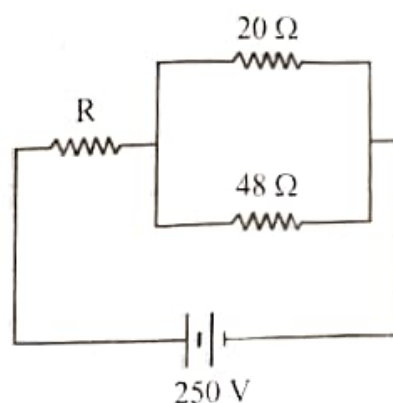


Fig. 1.12

1.6 In the given circuit shown in Fig. 1.13, calculate (a) the total current (b) current in 5 Ω and (c) the power dissipated in 6 Ω and 7 Ω .

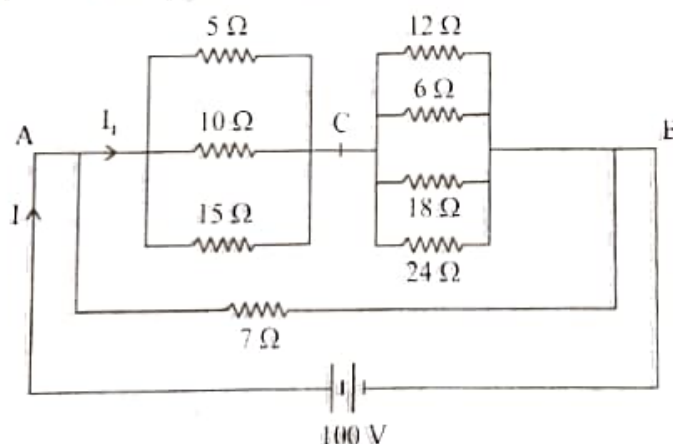


Fig. 1.13

Soln.

$$\text{a) } \frac{1}{R_{AC}} = \frac{1}{5} + \frac{1}{10} + \frac{1}{15} = \frac{11}{30} \Omega, \quad \therefore R_{AC} = 2.73 \Omega$$

$$\frac{1}{R_{CB}} = \frac{1}{12} + \frac{1}{6} + \frac{1}{18} + \frac{1}{24} = \frac{25}{72} \Omega, \quad \therefore R_{CB} = 2.88 \Omega$$

$$R_{ACB} = R_{AC} + R_{CB} = 2.73 + 2.88 = 5.61 \Omega$$

$$\text{The total resistance} = R_T = \frac{5.61 \times 7}{5.61 + 7} = 3.11 \, \Omega, \quad I = \frac{100}{3.11} = 32.15 \, \text{A}$$

$$\text{b) } I_1 = 32.15 \times \frac{7}{7 + 5.61} = 17.85 \, \text{A}, \quad E_{AC} = 17.85 \times R_{AC} = 17.85 \times 2.73 = 48.73 \, \text{V}$$

$$I_{5\Omega} = \frac{48.73}{5} = 9.75 \, \text{A}$$

$$\text{c) } E_{CB} = 100 - E_{AC} = 100 - 48.73 = 51.27 \, \text{V}, \quad P_{6\Omega} = \frac{E_{CB}^2}{6} = \frac{51.27^2}{6} = 438.1 \, \text{W}$$

$$P_{7\Omega} = \frac{E_{AB}^2}{7} = \frac{100^2}{7} = 1,428.57 \, \text{W}$$

1.7 A current of 30 A flows through two ammeters A_1 and A_2 connected in series. The p.d. across the two ammeters are 0.3 V and 0.6 V respectively. Find how the same current will divide when they are connected in parallel.

Soln.: Let R_1 and R_2 be the resistances of the ammeters A_1 and A_2 respectively.

$$30 R_1 = 0.3, \quad \therefore R_1 = 0.01 \, \Omega$$

$$30 R_2 = 0.6, \quad \therefore R_2 = 0.02 \, \Omega$$

The two ammeters are now connected in parallel as shown in Fig. 1.15.

$$I_1 = 30 \times \frac{0.02}{0.02 + 0.01} = 20 \, \text{A}$$

$$I_2 = 30 - 20 = 10 \, \text{A}$$

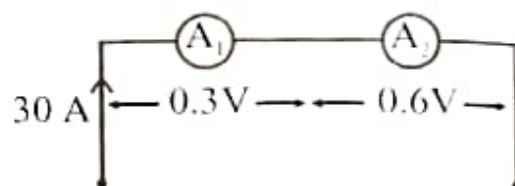


Fig. 1.14

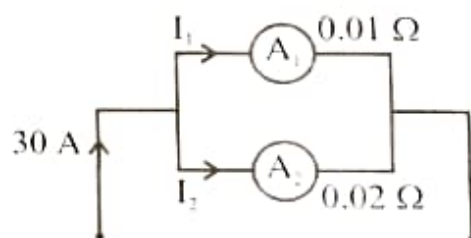


Fig. 1.15

1.8 A voltage of 200 V is applied to a tapped resistor of 500 Ω. Find the resistance between the tapping points connected to a load, needing 0.1 A at 25 V. Also calculate the total power consumed.

Soln.: Let the resistor be tapped between points B and C and x be the resistance between these points.

$$\therefore R_{BC} = x \, \Omega$$

$$\text{Then, } (1 - 0.1)x = 25 \quad \text{i.e.} \quad Ix - 0.1x = 25 \quad (1.14)$$

$$\text{Also, } I(500 - x) = 200 - 25 = 175 \quad \text{i.e.} \quad 500I - Ix = 175 \quad (1.15)$$

Adding equations (1.14) and (1.15), we get

$$500 I - 0.1 x = 200, \quad \text{or} \quad I = \frac{200 + 0.1x}{500} \quad (1.16)$$

Substituting I given by equation (1.16) in equation (1.14), we get

$$\frac{200 + 0.1x}{500} x - 0.1 x = 25$$

on simplification, we get

$$0.1 x^2 + 150 x - 12,500 = 0$$

$$\therefore x = \frac{-150 \pm \sqrt{150^2 + 4 \times 0.1 \times 12,500}}{2 \times 0.1} = 79.15 \, \Omega$$

(considering only the positive value)

Substituting this value in equation (1.14), we get, $I = 0.42 \, \text{A}$

Total power consumed $= 200 \times I = 200 \times 0.42 = 84 \, \text{watts}$

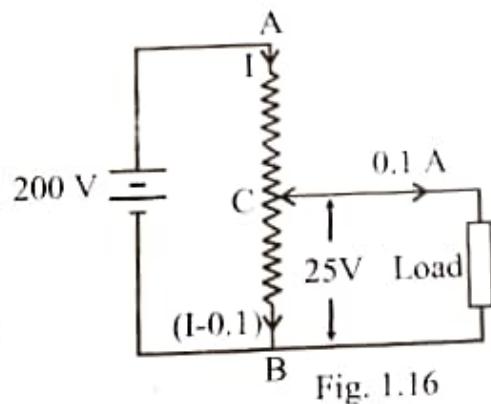


Fig. 1.16